Project 08-deb2

Hardware

ESP32 development board 2 Tact switch Jumper wire Filter capacitor

Connections

From GND and from 3V3 on ESP32 development board to both negative (blue) and positive rails of one side

From GPIO 'PUSH_00' to one side of Tact switch 0
From the other side of Tact switch to negative (blue) rail
From GPIO 'PUSH_01' to one side of Tact switch 1
From the other side of Tact switch to negative (blue) rail

Between both power supply rails (red and blue, a capacitor in order to filter 3V3 power supply

Please note, if one of tact switch is that marked as 'BOOT' or 'IOO' in board, connection must not be done and only must be defined as GPIO 0, as is defined PUSH_00 originally in platformio.ini

If user want to use more tact switches, please connect other as indicated and define GPIO's in platformio.ini

Software nodifications

If user add more switches, proceed as follows:

- 1. Connect each switch as stated in Connections.
- 2. Add GPIO number under build_flags in platformio.ini
- 3. Edit push.h and add symbolic name of each switch in enum
- 4. Edit push.cpp and add GPIO name in array pin
- 5. After that, always refer in your program using the symbolic name defined in *enum*

Important Notes

Please, remember that not all GPIOs may be used; consult Web document named *ESP32 Pinout Reference:* Which GPIO pins should you use?

Web documents

The simplest button debounce solution A Guide to debouncing, Part 2

ESP32 Pinout Reference: Which GPIO pins should you use?

debounce library github

e-tinkers/button